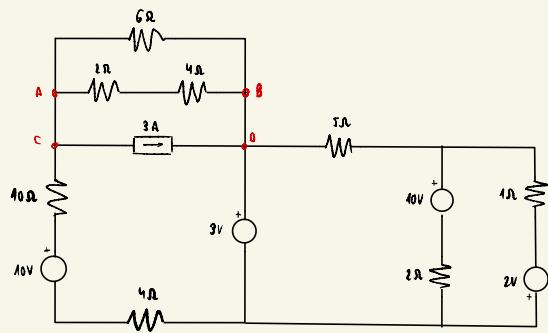


$$\begin{aligned} V_1 &= I_1 R_1 + (I_1 - I_2) R_3 = I_1 R_1 + I_1 R_3 - I_2 R_3 = I_1 (R_1 + R_3) - I_2 R_3 \\ V_2 &= I_2 R_2 + (I_2 - I_1) R_3 = I_2 R_2 + I_2 R_3 - I_1 R_3 = I_2 (R_2 + R_3) - I_1 R_3 \end{aligned} \quad \left. \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \begin{pmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{pmatrix} \right\}$$

$$I_1 = \frac{\begin{vmatrix} V_1 & -R_3 \\ V_2 & R_2 + R_3 \end{vmatrix}}{\begin{vmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{vmatrix}} \quad I_2 = \frac{\begin{vmatrix} R_1 + R_3 & V_1 \\ -R_3 & V_2 \end{vmatrix}}{\begin{vmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{vmatrix}} \rightarrow \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \begin{pmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{pmatrix}$$



$$R_{AB} = 2 + 4 = 6 \Omega$$


$$\frac{1}{R_{CD}} = \frac{1}{6} + \frac{1}{6} = \frac{1}{3} \quad ; \quad R_{CD} = 3 \Omega$$



$$V_{ce} - RI = 9 - 3 = 6V$$

$$\begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} \rightarrow \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 10+2+1 & 0 & 0 \\ 10-2 & 2+2 & 2 \\ 0 & 2 & 3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

$$I_1 = \frac{\begin{vmatrix} 0 & 0 \\ 10 & 2+2 \end{vmatrix}}{\begin{vmatrix} 10 & 2+2 & 2 \\ 10-2 & 0 & 0 \\ 0 & 2 & 3 \end{vmatrix}} = 0,94A$$
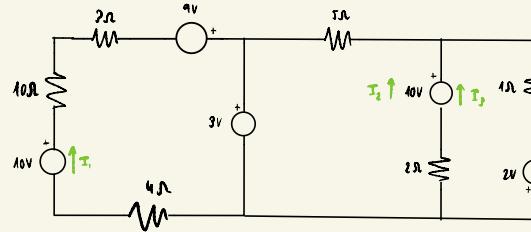
$$P_1 = 4 \cdot (0,94)^2 = 3,58W \text{ W}$$



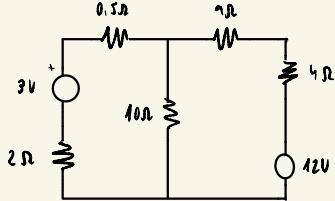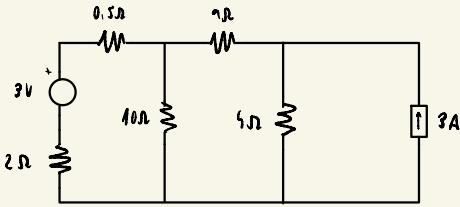


$$V = RI = 4 \cdot 3 = 12V$$

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \rightarrow \begin{pmatrix} 3 \\ 12 \end{pmatrix} = \begin{pmatrix} 40+2+0.5 & 10 \\ 10 & 40+9+4 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$I_1 = \frac{\begin{vmatrix} 3 & 10 \\ 12 & 23 \end{vmatrix}}{\begin{vmatrix} 42.5 & 10 \\ 16.5 & 23 \end{vmatrix}}$$

$$I_2 = \frac{\begin{vmatrix} 42.5 & 10 \\ 16.5 & 23 \end{vmatrix}}{\begin{vmatrix} 42.5 & 40 \\ 16.5 & 23 \end{vmatrix}}$$

## Método de tensiones de nodos

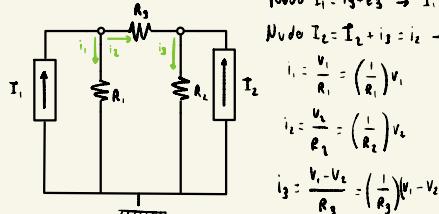


$$\begin{aligned}
 \text{Nodo } T_1: i_3 + i_2 &\rightarrow I_1 = \left(\frac{1}{R_1}\right)V_1 + \left(\frac{1}{R_3}\right)(V_1 - V_2) \rightarrow I_1 = G_1 V_1 + G_2 V_1 - G_3 V_2 \\
 \text{Nodo } T_2: I_2 + i_2 &= i_1 \rightarrow I_2 = i_1 - i_3 \rightarrow I_2 = \left(\frac{1}{R_2}\right)V_2 - \left(\frac{1}{R_3}\right)(V_1 - V_2) \rightarrow I_2 = G_2 V_2 - G_3 V_1 + G_3 V_2
 \end{aligned} \quad \left. \begin{array}{l} I_1 = V_1(G_1 + G_3) - V_2 G_3 \\ I_2 = -V_1 G_3 + V_2(G_2 + G_3) \end{array} \right\}$$

$$I_1 = \frac{V_1}{R_1} = \left(\frac{1}{R_1}\right)V_1$$

$$i_2 = \frac{V_2}{R_2} = \left(\frac{1}{R_2}\right)V_2$$

$$i_3 = \frac{V_1 - V_2}{R_3} = \left(\frac{1}{R_3}\right)(V_1 - V_2)$$
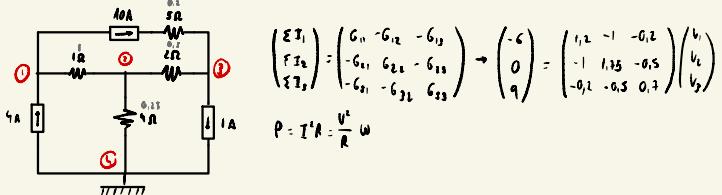
$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} G_1 + G_3 & -G_3 \\ -G_3 & G_2 + G_3 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$



$$\begin{pmatrix} \Sigma I_1 \\ \Sigma I_2 \\ \Sigma I_3 \end{pmatrix} = \begin{pmatrix} G_{11} - G_{12} - G_{13} \\ -G_{11} + G_{22} - G_{13} \\ -G_{11} - G_{22} + G_{33} \end{pmatrix} \rightarrow \begin{pmatrix} -6 \\ 0 \\ 9 \end{pmatrix} = \begin{pmatrix} 1,2 & -1 & -0,2 \\ -1 & 1,35 & -0,5 \\ -0,2 & -0,5 & 0,3 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix}$$


$$P = I^T R = \frac{V^2}{R}$$

## 0. INGRESO AL R


$$V_R = \frac{\begin{vmatrix} -1,2 & -1 & -0,2 \\ -1 & 1,35 & -0,5 \\ -0,2 & -0,5 & 0,3 \end{vmatrix}}{\begin{vmatrix} 1,2 & -1 & -0,2 \\ -1 & 1,35 & -0,5 \\ -0,2 & -0,5 & 0,3 \end{vmatrix}}$$

$$P = \frac{(V_R)^2}{R} W$$

## Método de superposición

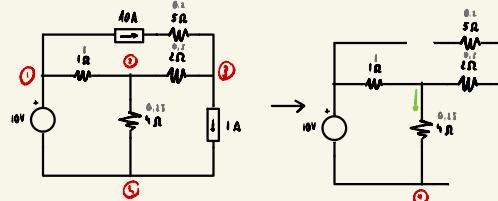
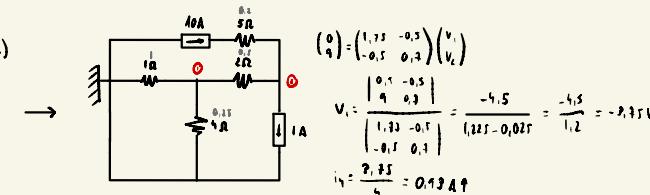
$$i_A = \frac{10}{\delta} = 2 \text{ A J (F. tensión)}$$



$$\begin{pmatrix} 0 \\ 1 \end{pmatrix} = \begin{pmatrix} 1.75 & -0.5 \\ -0.5 & 0.2 \end{pmatrix} \begin{pmatrix} V_L \\ V_L \end{pmatrix}$$



$$V_L = \frac{\begin{vmatrix} 1 & -0.5 \\ 1 & 0.2 \end{vmatrix}}{\begin{vmatrix} 1.75 & -0.5 \\ -0.5 & 0.2 \end{vmatrix}} = \frac{-4.5}{1.225 - 0.025} = \frac{-4.5}{1.2} = -3.75 \text{ V}$$

$$i_A = \frac{2.75}{0.1} = 0.1375 \text{ A}$$

$$I_{TH} = 2A(1) - 0.1375A(0) = 1.0125 \text{ A (L)}$$


$$P = i^2 R = (1.0125)^2 \cdot 0.1 = \dots$$

## Método de Thevenin y Norton

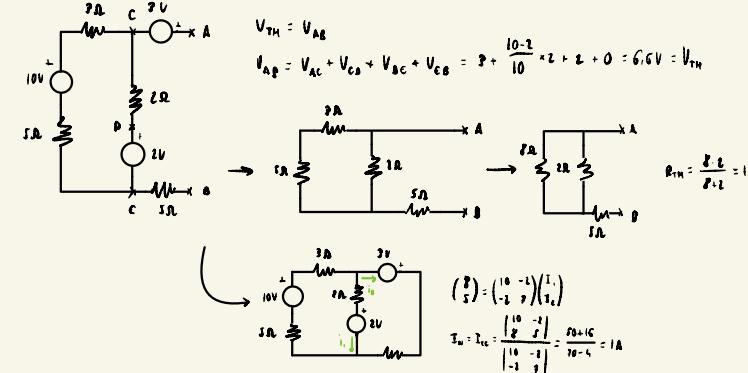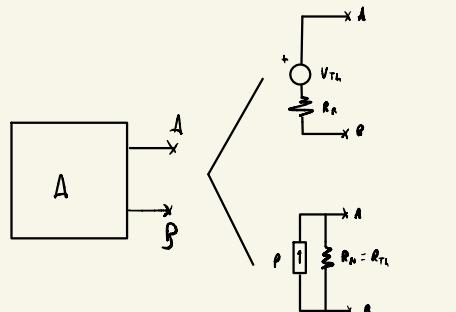

$$\begin{pmatrix} 0 \\ 1 \end{pmatrix} = \begin{pmatrix} 10 & -1 \\ -1 & 1 \end{pmatrix} \begin{pmatrix} V_{AB} \\ V_{AB} \end{pmatrix}$$
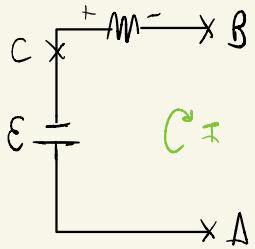
$$I_{TH} = I_{AB} = \frac{\begin{vmatrix} 10 & -1 \\ -1 & 1 \end{vmatrix}}{\begin{vmatrix} 10 & -1 \\ -1 & 1 \end{vmatrix}} = \frac{10+1}{10-1} = \frac{11}{9} = 1.222 \text{ A}$$




$$I_{CL} = \frac{E}{R} \quad E = I_{CC} R$$

$\longleftrightarrow$


$$R = r$$

$$V_{CB} = IR$$

$$V_{BC} = -IR$$

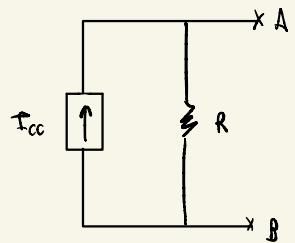


$$I_{CC} = \frac{E}{R}$$

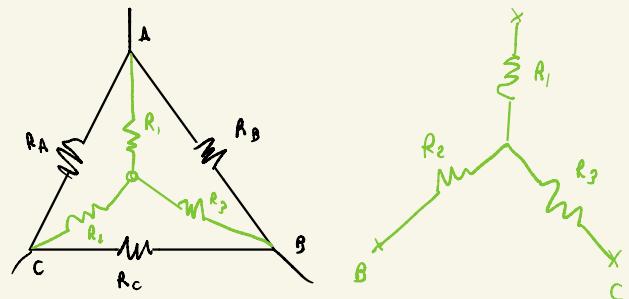

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$
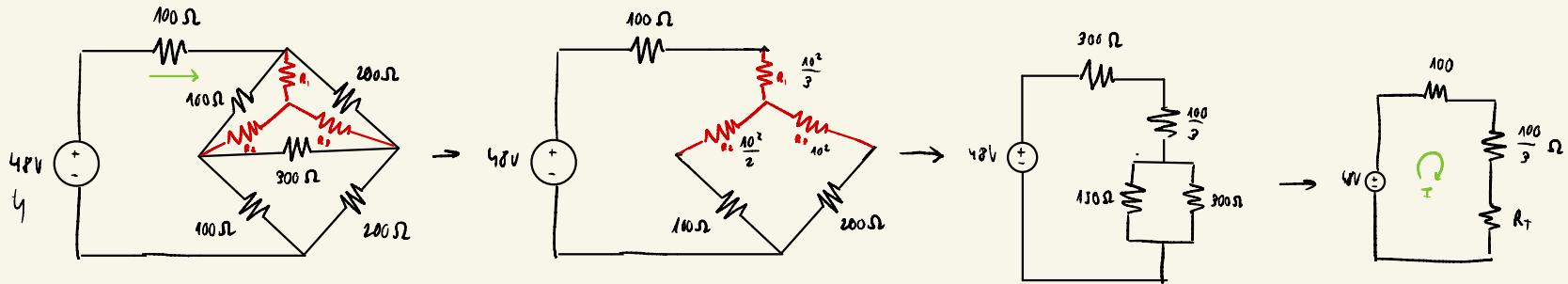
$$R_3 = \frac{R_B R_C}{R_A + R_B + R_C}$$



$$R_1 = \frac{2 \cdot 10^4}{6 \cdot 10^2} = \frac{1}{3} \cdot 10^2$$


$$R_2 = \frac{3 \cdot 10^4}{6 \cdot 10^2} = \frac{1}{2} \cdot 10^2$$

$$R_3 = \frac{6 \cdot 10^4}{6 \cdot 10^2} = 10^2$$

$$I = \frac{\Sigma E - \Sigma E' }{\Sigma R} = \frac{48}{100/3} = \frac{48 \cdot 3}{100}$$

$$R_T = \frac{150 \cdot 200}{450} = \frac{4500}{45} = 100 \Omega$$
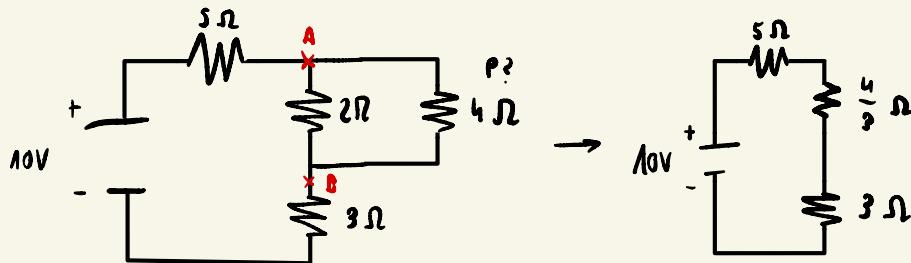
$$R_T = 200 + \frac{100}{3} = \frac{700}{3}$$




$$I = \frac{E}{\sum R} = \frac{10}{5+3+\frac{4}{3}} = \frac{10 \cdot 3}{18+9+4} = \frac{30}{28} \text{ A}$$

$$V_{AB} = R_{eq} \cdot \frac{30}{28} = \frac{4}{3} \cdot \frac{30}{28} = \frac{40}{28}$$

$$I = \frac{V}{R} = \frac{40/28}{4} = \frac{10}{28} \text{ A}$$

$$R = I^2 R = 4 \left( \frac{10}{28} \right)^2 \text{ W}$$

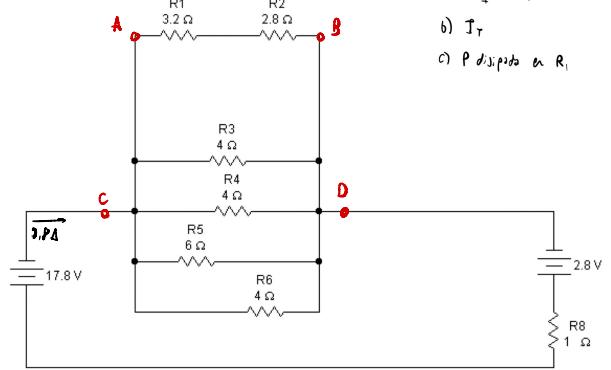9.- Completar el siguiente cuadro con el voltaje, la intensidad de corriente y la potencia eléctrica disipada por cada resistencia: a)  $R_{eq}$  del paralelo



$$a) R_{eq} = 2.8 + 3.2 = 6 \Omega$$

$$R_{eq} = \frac{1}{R_{eq}} = \frac{1}{\frac{1}{6} + \frac{1}{4} + \frac{1}{4} + \frac{1}{6} + \frac{1}{6}} = \frac{2}{6} + \frac{2}{3} = \frac{13}{12} \quad R_{eq} = \frac{12}{13} \Omega$$

$$b) I_T = \frac{\Delta E - E' E}{R_{eq}} = \frac{17.8 - 2.8}{1 + \frac{12}{13}} = \frac{15}{25/13} = 7.8 A$$

$$c) V_{eq} = I_T R_7 = 7.8 \cdot \frac{12}{13} = 7.2 V$$

$$I_2 = \frac{V_{eq}}{R_{eq}} = \frac{7.2}{6} A$$

$$P_1 = I^2 R_1 = \left(\frac{7.2}{6}\right)^2 \cdot 2.2 = 9.6 W$$

