
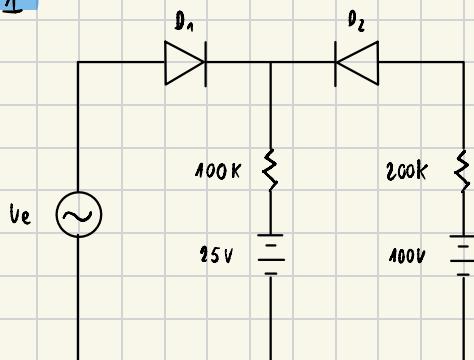


**DIODOS**

1

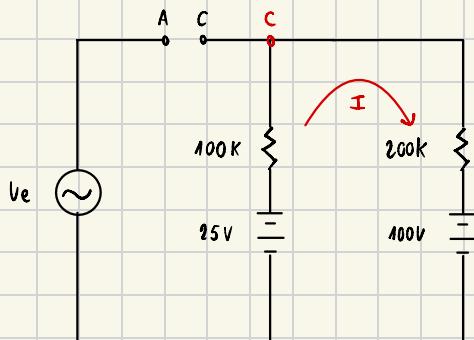

D<sub>1</sub> PL D<sub>2</sub> ON:



$$V_A = V_e$$

$$V_C = 100 + 200K I_2$$

$$-75 = 300K I_2 ; \quad I_2 = \frac{-75}{300K}$$


$$V_C = 100 - \frac{150}{3} = 50V$$

$$V_A - V_C = V_e - 50$$

$V_e > 50 \quad D_1 \text{ ON} \quad D_2 \text{ ON}$

$V_e < 50 \quad D_1 \text{ OFF} \quad D_2 \text{ ON}$

$D_1$  PL  $D_2$  OFF:

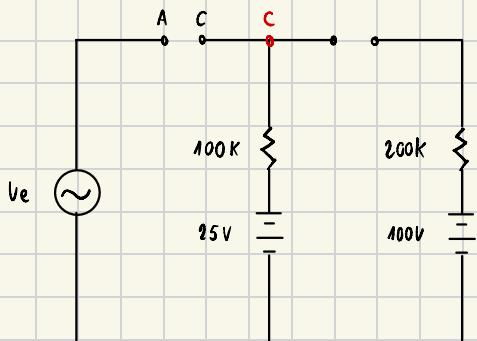

$$v_A = v_e$$


$$v_c = 25 + 100kI^0$$

$$v_A - v_C = v_e - 25$$

$v_e > 25 \quad D_1 \text{ ON} \quad D_2 \text{ OFF}$

$v_e < 25 \quad D_1 \text{ OFF} \quad D_2 \text{ OFF}$

$D_1$  ON  $D_2$  PL:

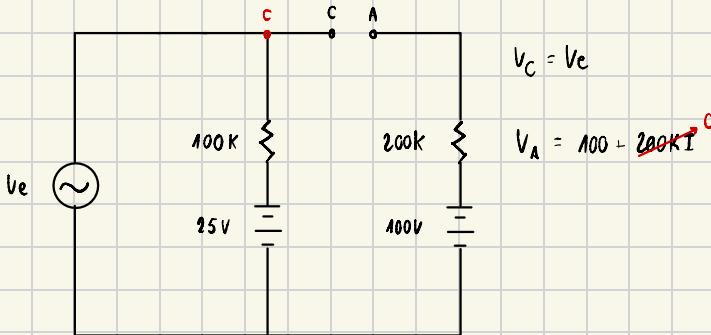

$$v_C = v_e$$


$$v_A = 100 - 200kI^0$$

$$v_A - v_C = 100 - v_e \quad 100 > v_e$$

$v_e > 100 \quad D_1 \text{ ON} \quad D_2 \text{ OFF}$

$v_e < 100 \quad D_1 \text{ ON} \quad D_2 \text{ ON}$

$D_1$  OFF  $D_2$  ON:

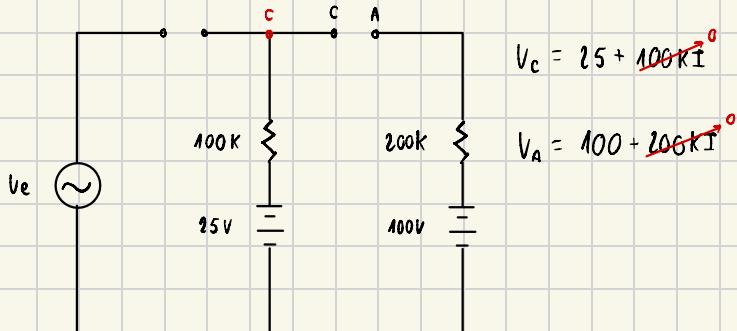

$$V_A - V_C = 100 - 25 = 75V$$

$D_1$  OFF  $\rightarrow D_2$  ON

$\left\{ \begin{array}{l} V_e > 25 \quad D_1 \text{ ON} \quad D_2 \text{ OFF} \\ V_e < 25 \quad D_1 \text{ OFF} \quad D_2 \text{ OFF} \end{array} \right.$

$\left\{ \begin{array}{l} V_e > 50 \quad D_1 \text{ ON} \quad D_2 \text{ ON} \\ V_e < 50 \quad D_1 \text{ OFF} \quad D_2 \text{ ON} \end{array} \right.$

$\left\{ \begin{array}{l} V_e > 100 \quad D_1 \text{ ON} \quad D_2 \text{ OFF} \\ V_e < 100 \quad D_1 \text{ ON} \quad D_2 \text{ ON} \end{array} \right.$


•  $D_1$  OFF  $\rightarrow D_2$  ON

INCOMPATIBLE

$D_1$ OFF	$D_1$ ON	$D_1$ ON
$D_2$ ON	$D_2$ ON	$D_2$ OFF



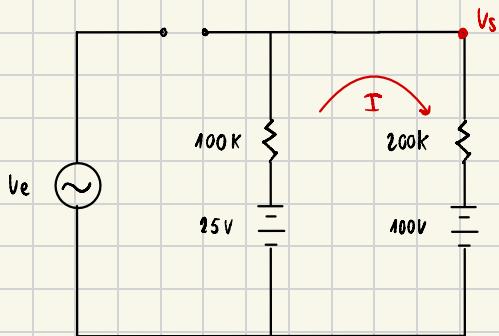$V_e < 50 \text{ V}$  ( $D_1$  off,  $D_2$  on)




$$V_s = 100 + 200kI$$

$$25 - 100 = 300kI ; I = \frac{-75}{300k}$$

$$V_s = 100 + 200k \frac{-75}{300k} = 100 - 50 = 50 \text{ V}$$

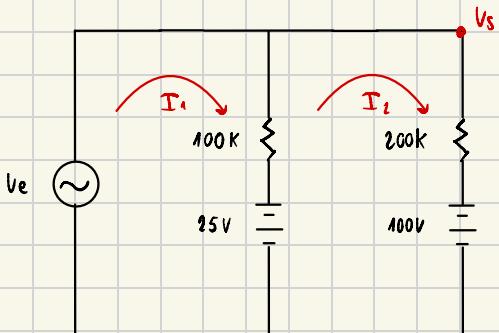$50 < V_e < 100$  ( $D_1$  on,  $D_2$  on)



$$V_e - 25 = 100kI_1 - 100kI_2$$

$$25 - 100 = 300kI_2 - 100kI_1$$



$$V_e - 100 = 200kI_2$$

$$I_2 = \frac{V_e - 100}{200k}$$


$$\frac{V_e - 100}{200k}$$

$$V_s = 100 + 200kI = 100 + 200k \frac{V_e - 100}{200k} = V_e$$


$V_e > 100$  ( $D_1$  ON,  $D_2$  OFF)

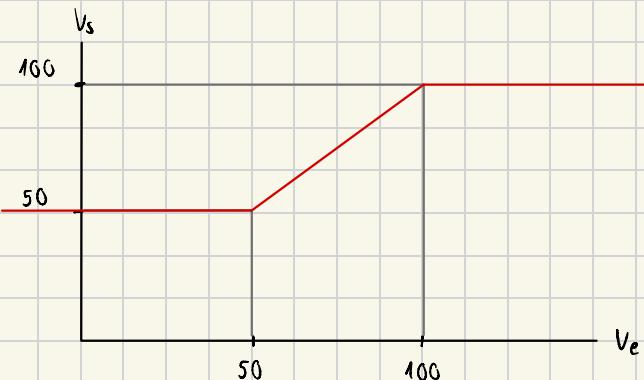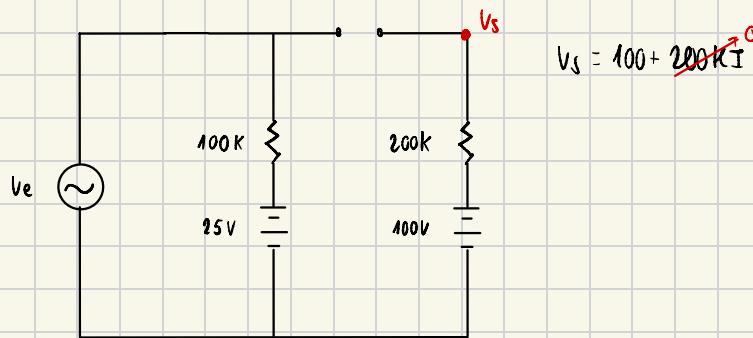

2

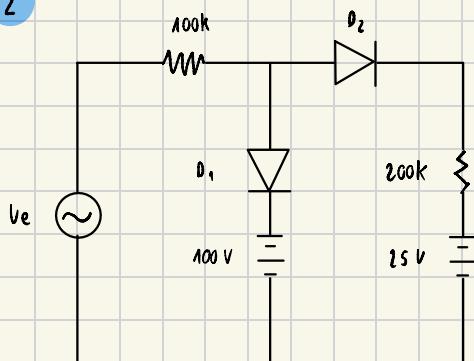

D<sub>1</sub> PL D<sub>2</sub> ON:

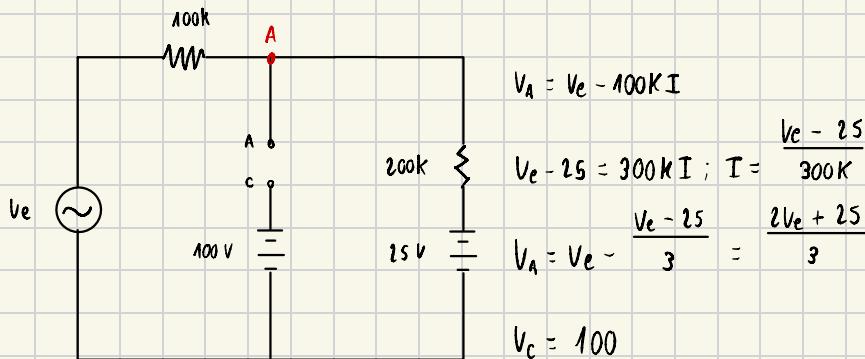


$$V_A - V_C = \frac{2V_e + 25}{3} - 100 = \frac{2V_e - 275}{3}$$

$V_e > 137,5 \text{ V } D_1 \text{ ON } D_2 \text{ ON}$

$V_e < 137,5 \text{ V } D_1 \text{ Off } D_2 \text{ ON}$

$D_1$  PL  $D_2$  ON:

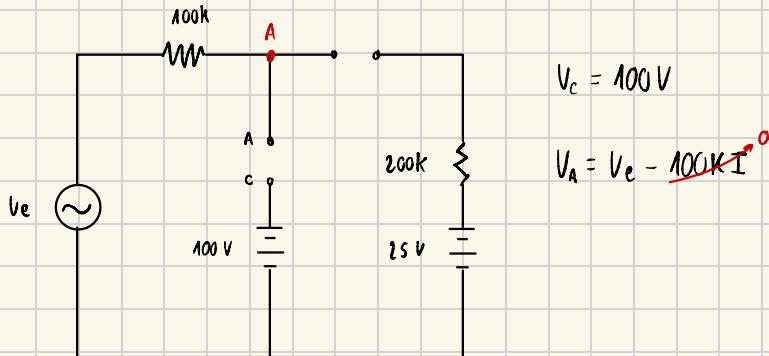


$$V_A - V_c = V_e - 100$$

$V_e > 100\text{ V}$   $D_1$  ON  $D_2$  OFF

$V_e < 100\text{ V}$   $D_1$  OFF  $D_2$  OFF


$D_1$  ON  $D_2$  PL:

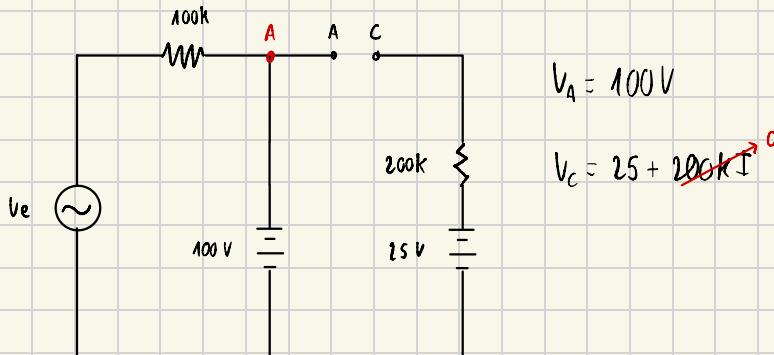

$$V_A - V_c = 100 - 25 = 75\text{ V}$$

$D_1$  ON  $\rightarrow$   $D_2$  ON

$D_1$  OFF  $D_2$  ON

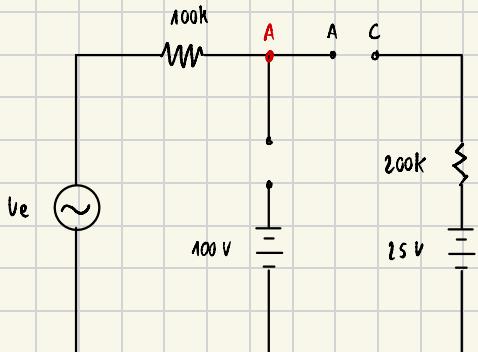

$$V_A = V_e + 100\text{k} I$$

$$V_C = 25 + 200\text{k} I$$

$$V_A - V_C = V_e - 25$$

$V_e > 25\text{V}$   $D_1$  OFF  $D_2$  ON

$V_e < 25\text{V}$   $D_1$  OFF  $D_2$  OFF

{  $V_e > 25\text{V}$   $D_1$  OFF  $D_2$  ON

{  $V_e < 25\text{V}$   $D_1$  OFF  $D_2$  OFF

{  $V_e > 100\text{V}$   $D_1$  ON  $D_2$  OFF

{  $V_e < 100\text{V}$   $D_1$  OFF  $D_2$  OFF


{  $V_e > 137,5\text{V}$   $D_1$  ON  $D_2$  ON

{  $V_e < 137,5\text{V}$   $D_1$  OFF  $D_2$  ON


•  $D_1$  ON  $\rightarrow$   $D_2$  ON

INCOMPATIBLE


$D_1$ OFF	$D_1$ OFF	$D_1$ ON
$D_2$ OFF	$D_2$ ON	$D_2$ ON

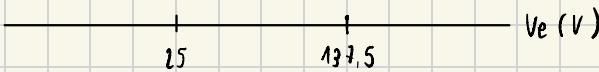


$v_e < 25V$  ( $D_1$  OFF,  $D_2$  OFF)

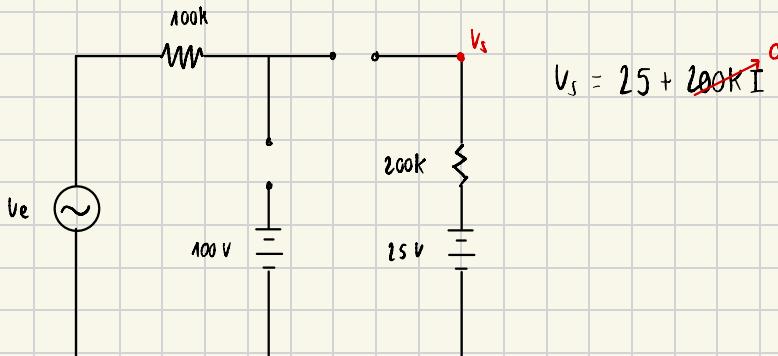

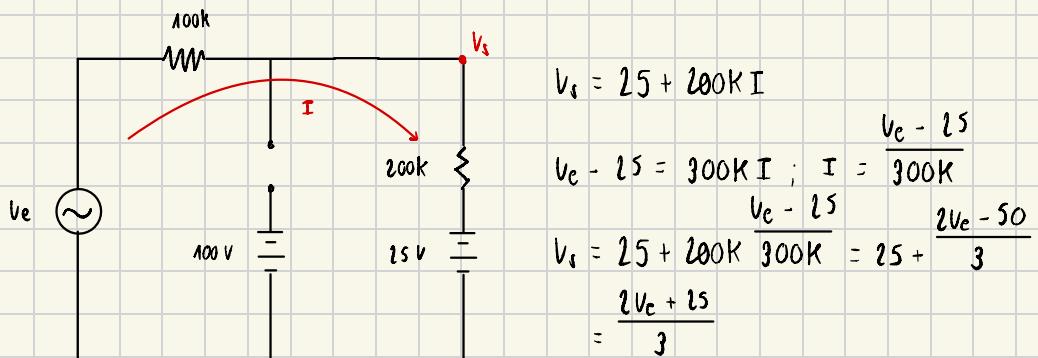$25 < v_e < 137,5V$  ( $D_1$  OFF,  $D_2$  ON)


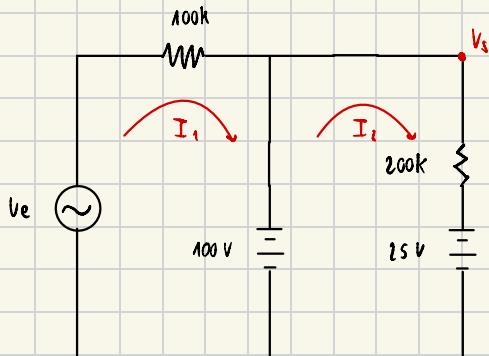
$$V_e > 137.5 \text{ V} (\text{D}_1 \text{ ON}, \text{D}_2 \text{ ON})$$




$$V_s = 25 + 200K I_2$$


$$V_e - 100 = 100K I_1$$

$$100 - 25 = 200K I_2 ; I_2 = \frac{75}{200K}$$

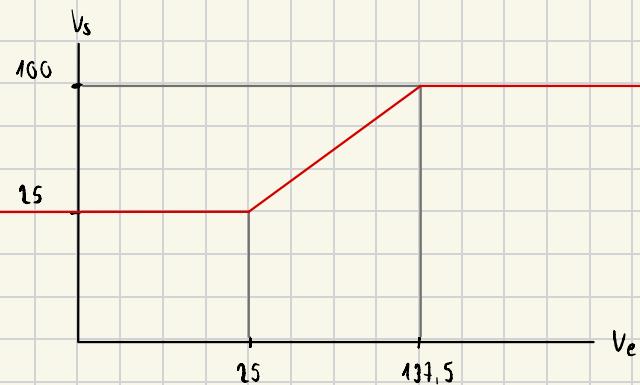
$$V_s = 25 + 200K \frac{75}{200K} = 100 \text{ V}$$



3

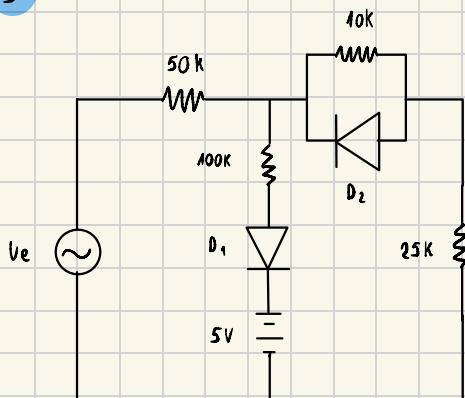

D1 PL D2 ON

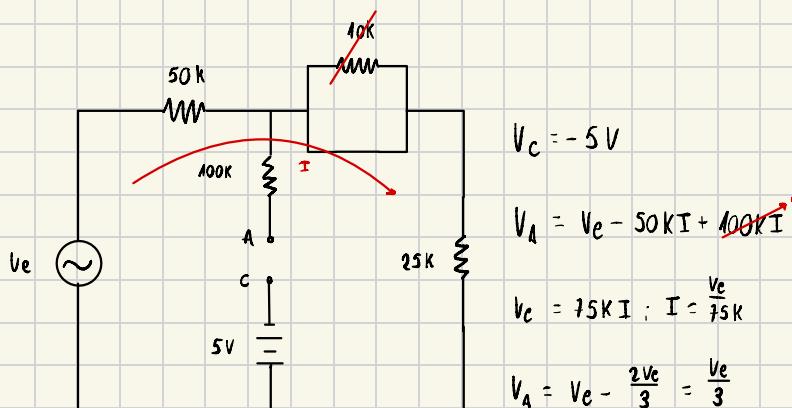


$$V_A - V_C = \frac{V_e}{3} + 5 = \frac{V_e + 15}{3}$$

$$V_e > -15V \quad D_1 \text{ OFF} \quad D_2 \text{ ON}$$

$$V_e < -15V \quad D_1 \text{ ON} \quad D_2 \text{ ON}$$

D1 PL D2 off

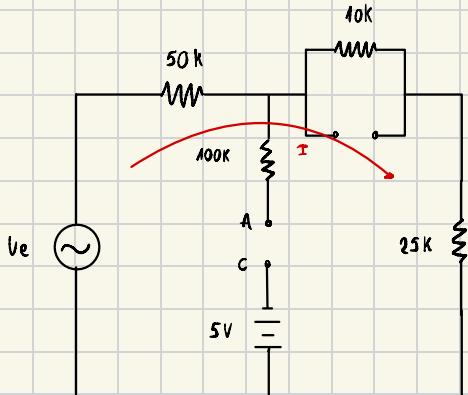

$$V_C = -5V$$

$$V_A = V_e - 50kI + \cancel{100kI}$$

$$V_C = 85kI; I = \frac{V_e}{85k}$$


$$V_A = V_e - \frac{50}{85} V_e = \frac{7}{17} V_e$$

$$V_A - V_C = \frac{7}{17} V_e + 5 = \frac{7V_e + 85}{17}$$

$$V_e > -12,143V \quad D_1 \text{ ON} \quad D_2 \text{ off}$$

$$V_e < -12,143V \quad D_1 \text{ off} \quad D_2 \text{ off}$$

D1 ON D2 PL

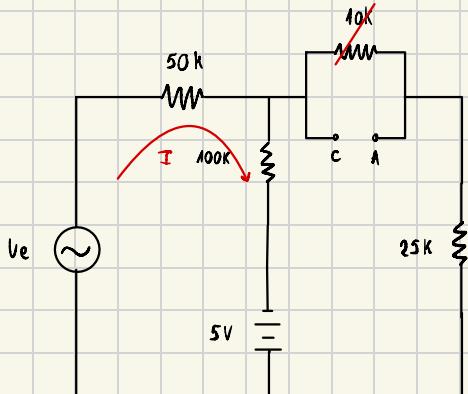

$$V_C + 5 = 150kI; I = \frac{V_e + 5}{150k}$$

$$V_C = 50kI - V_e = \frac{V_e + 5}{3} - V_e = \frac{5 - 2V_e}{3}$$


$$V_A = \cancel{25kI} = 0$$

$$V_A - V_C = \frac{2V_e - 5}{3}$$

$$V_e > 2,5V \quad D_1 \text{ ON} \quad D_2 \text{ ON}$$

$$V_e < 2,5V \quad D_1 \text{ ON} \quad D_2 \text{ off}$$

D1 OFF D2 PL

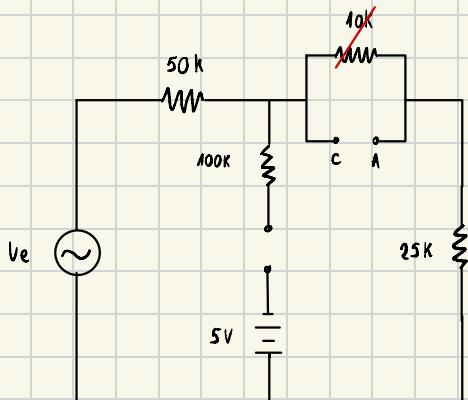

$$V_A = \cancel{SOKI}^0 - V_e$$

$$V_r = 25KI^0 = 0$$

$$V_A - V_C = -V_e \quad V$$

$V_e > 0$        $D_1$  off     $D_2$  off

$V_e < 0$       D<sub>1</sub> off    D<sub>2</sub> on

$$V_c > -15V \quad D_1 \text{ off} \quad D_2 \text{ on}$$

$$V_E < -15V \quad D_1 \text{ ON} \quad D_2 \text{ ON}$$

$V_e > -12.143V$   $D_1$  ON  $D_2$  OFF  
incompatibles

$V_e < -12.143V$  D<sub>1</sub> OFF D<sub>2</sub> OFF

$$V_c > 0 \quad \rho_1 \text{ off} \quad \rho_2 \text{ off}$$


$$V_0 < 0 \quad \rho_1 \text{ off} \quad \rho_1 \text{ on}$$

incompatible


$$V_C > 2,5V \quad D_1 \text{ ON } D_2 \text{ ON } \swarrow$$

$V_C < 2.5V$  D<sub>1</sub> ON D<sub>2</sub> OFF


COGELOS LOS  
EXTREMOS

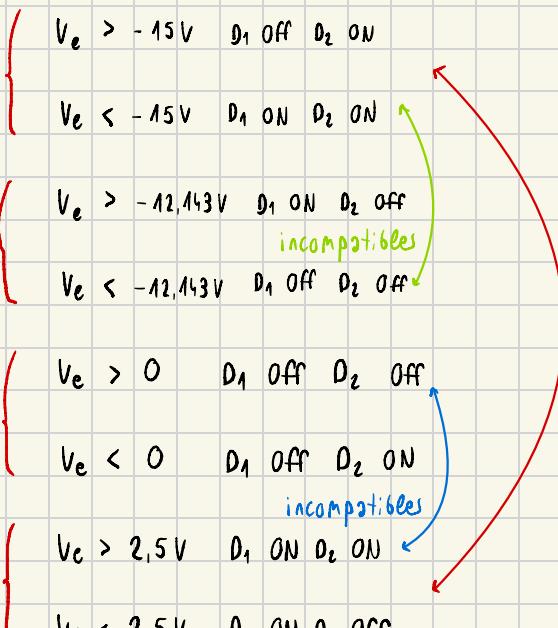

D <sub>1</sub> , OFF	D <sub>1</sub> , ON	D <sub>1</sub> , ON
D <sub>2</sub> , ON	D <sub>2</sub> , ON	D <sub>2</sub> , OFF

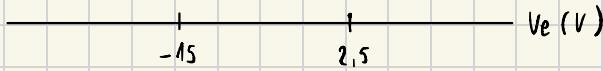
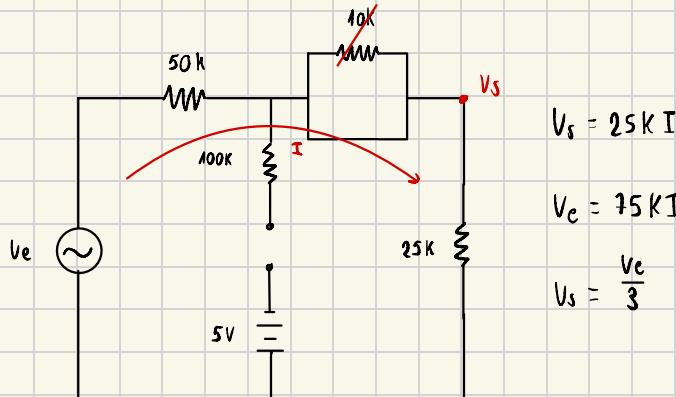
$$V_e < -1.5V \quad (D_1 \text{ OFF}, D_2 \text{ ON})$$




$$V_s = 25kI$$

$$V_e = 75kI; \quad I = \frac{V_e}{75k}$$

$$V_s = \frac{V_e}{3}$$
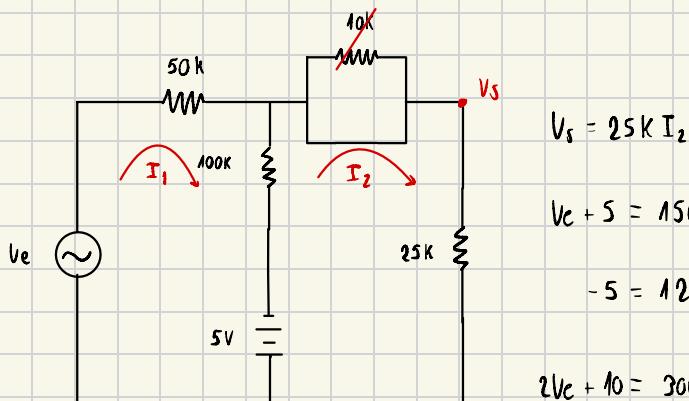
$$-1.5 < V_e < 2.5V \quad (D_1 \text{ ON}, D_2 \text{ ON})$$



$$V_s = 25kI_2$$


$$\begin{aligned} V_e + 5 &= 150kI_1 - 100kI_2 \\ -5 &= 125kI_2 - 100kI_1 \end{aligned} \quad \left. \begin{array}{l} \times 2 \\ \times 3 \end{array} \right\}$$

$$\begin{aligned} 2V_e + 10 &= 300kI_1 - 200kI_2 \\ -15 &= 375kI_2 - 300kI_1 \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\}$$

$$2V_e - 5 = 175kI_2; \quad I_2 = \frac{2V_e - 5}{175k}$$

$$V_s = 25kI_2 = \frac{2V_e - 5}{7}$$

$V_e > 2,5V$  ( $D_1$  ON,  $D_2$  OFF)

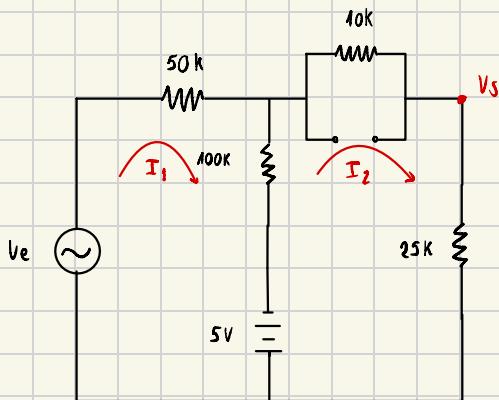

$$V_s = 25K I_2$$

$$V_e + 5 = 150K I_1 - 100K I_2 \quad \left. \right\} \times 2$$


$$5 = 135K I_2 - 100K I_1 \quad \left. \right\} \times 3$$

$$2V_e + 10 = 300K I_1 - 200K I_2 \quad \left. \right\}$$

$$2V_e - 5 = 205K I_1; \quad I_1 = \frac{2V_e - 5}{205K} \quad -15 = 405K I_2 - 300K I_1$$

$$V_s = 25K I_2 = 25K \frac{2V_e - 5}{205K} = \frac{10V_e - 25}{41}$$

$V_s$

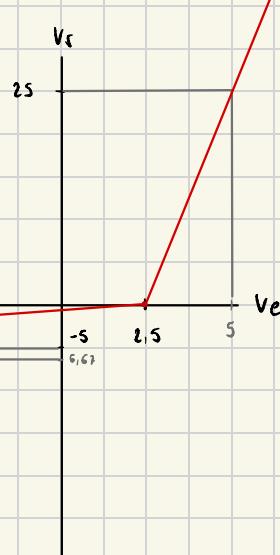


-10      -15

-5

6,67



2,5

5

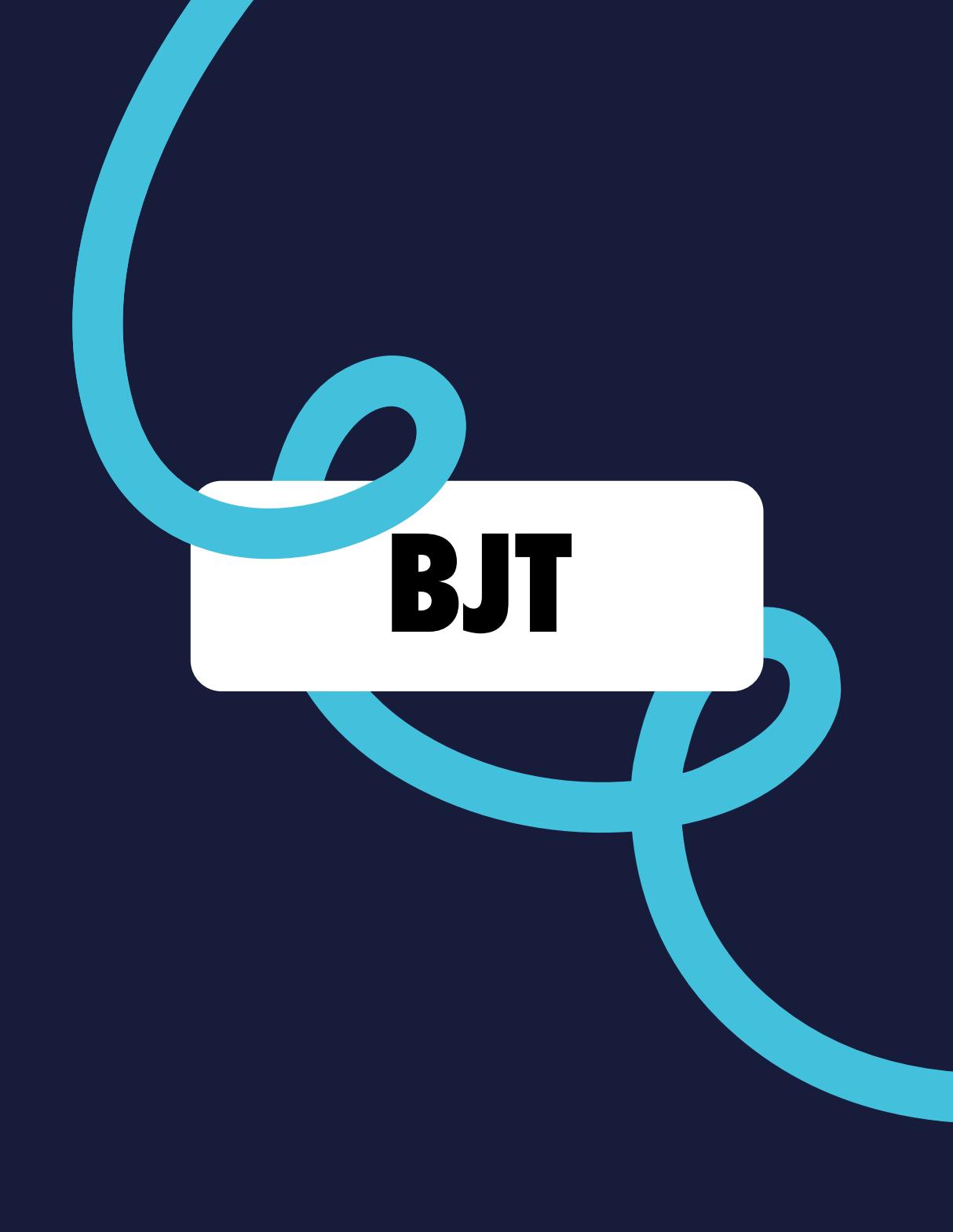


**BJT**

## Resistencias?

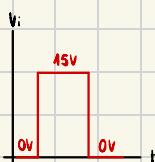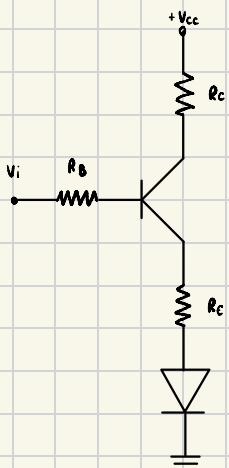
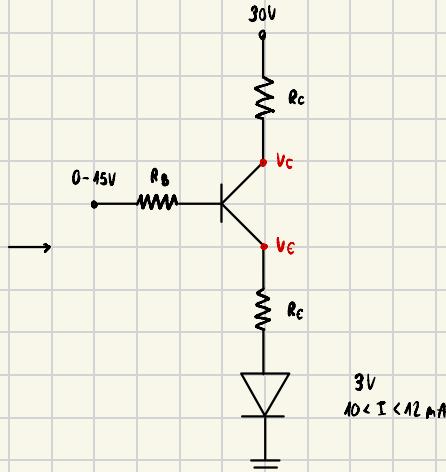
$$\begin{aligned} V_{CC} &= 30V \\ V_{eod} &= 3V \\ 10 \text{ mA} &< I_{eod} < 12 \text{ mA} \\ \beta &= 200 \end{aligned}$$



Suponemos  $I_e = 10 \text{ mA}$  (SAT)

$$\left. \begin{aligned} V_{CC} &= R_C I_C + V_C \\ V_C &= V_{CE} + V_E + V_{eod} \end{aligned} \right\} V_{CC} = R_C I_C + V_{CE} + V_E + V_{eod}$$

$$\left. \begin{aligned} I_E &= I_C + I_B \\ I_C &= I_B \beta \end{aligned} \right\} I_E = I_B \beta + I_B = I_B (\beta + 1) ; I_B = \frac{I_E}{\beta + 1} = \frac{10}{201} \text{ mA}$$

$$I_C = \frac{10}{201} \cdot 200 = \frac{2000}{201} \text{ mA}$$

$$V_C = R_C I_E = \frac{R_C}{\beta} I_E = \frac{R_C}{\beta} (I_C + I_B) = \frac{R_C}{\beta} \frac{2010}{201} = \frac{10}{\beta} R_C$$

$$V_{CC} = R_C I_C + V_{CE} + V_E + V_{eod} ; 30 = \frac{2000}{201} R_C + 0,2 + \frac{10 R_C}{\beta} + 3$$

$$\left( \frac{2000}{201} + \frac{10}{\beta} \right) R_C = 30 - 0,2 - 3 ; \frac{10010}{201} R_C = 26,8 ; R_C = 2,0883 \text{ k}\Omega$$

$$R_C = \frac{R_C}{\beta} = 0,5221 \text{ k}\Omega$$

$$\left. \begin{array}{l} V_{BB} = R_B I_B + V_B \\ V_B = V_{BE} + V_E - V_{LED} \end{array} \right\} V_{BB} = R_B I_B + V_{BE} + R_E I_E - V_{LED}$$


$$V_{BB} = R_B I_B + V_{BE} + R_E I_E - V_{LED}; \quad R_B I_B = V_{BB} - V_{BE} - R_E I_E - V_{LED}$$

$$R_B = \frac{V_{BB} - V_{BE} - R_E I_E - V_{LED}}{I_B} = \frac{15 - 0,7 - 0,5221 \cdot 10^{-3}}{\frac{10}{201}}$$

$$R_B = 122,1879 \text{ k}\Omega$$

2

**$V_C$  vs.  $V_{BB}$**

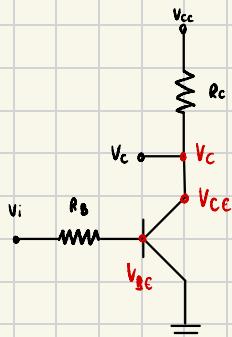

$$V_{CC} = 5V$$

$$R_C = 0.82 \text{ k}\Omega$$

$$R_B = 68 \text{ k}\Omega$$

$$h_{FE} = \beta = 125$$


$V_{CE} = 0.2 \text{ V} \rightarrow \text{SAT}$

$V_{BE} = 0.7 \text{ V} \rightarrow \text{CORTE}$

$$\left. \begin{array}{l} V_{CC} = I_C R_C + V_C \\ V_C = V_{CE} + V_E \\ R_C = 0 \rightarrow V_E = 0 \end{array} \right\} V_{CC} = I_C R_C + V_C ; I_C = \frac{V_{CC} - V_C}{R_C} = \frac{5 - 0.2}{0.82} = 5.8537 \text{ mA}$$


$$I_C = I_B \beta ; I_B = \frac{I_C}{\beta} = \frac{5.8537}{125} = 0.0468 \text{ mA}$$
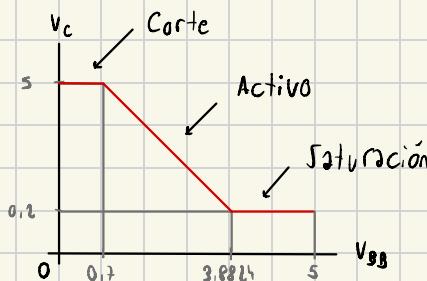
$$\left. \begin{array}{l} V_{BB} = I_B R_B + V_B \\ V_B = V_{BE} + V_E \end{array} \right\} V_{BB} = I_B R_B + V_B = 0.0468 \cdot 68 + 0.7 = 3.8824 \text{ V}$$



3

### V<sub>CE</sub> VS. V<sub>BB</sub>

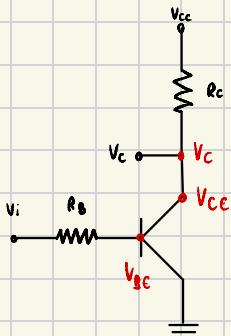

$$V_{CC} = 12 \text{ V}$$

$$R_C = 1,2 \text{ k}\Omega$$

$$R_B = 100 \text{ k}\Omega$$

$$\beta = 150$$


\* Gráfico:  $V_{BB_{max}} = 8 \text{ V}$

$$\left. \begin{array}{l} V_{CC} = I_C R_C + V_C \\ V_C = V_{CE} + R_E I_E \end{array} \right\}$$

$$V_{CC} = I_C R_C + V_{CE} ; I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{12 - 0,2}{1,2} = 9,8333 \text{ mA}$$


$$I_C = I_B \beta ; I_E = \frac{I_C}{\beta} = \frac{9,8333}{150} = 0,6556 \text{ mA}$$
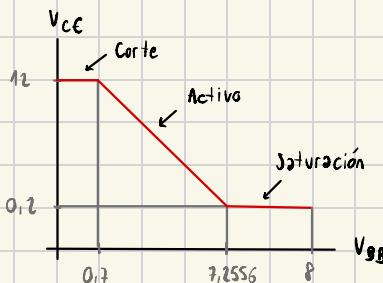
$$V_{BB} = I_E R_B + V_{BE} = 0,6556 \cdot 100 + 0,7 = 7,2556 \text{ V}$$



4

## Resistencias ?

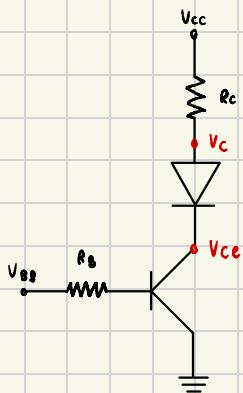

$$V_{ceo} = 2V$$

$$I_{ceo} > 8mA$$

$$\beta = 250$$

$$V_{CC} = 12V$$

\* Gráfico:  $V_{BB\max} = 10V$

$$V_{CC} = I_c R_C + V_{ceo} + V_{ce} + V_e^o ; \quad R_C = \frac{V_{CC} - V_{ceo} - V_{ce}}{I_c} = \frac{12 - 2 - 0,2}{8}$$

$$R_C = 1,225 \text{ k}\Omega$$

$$I_c = I_B \beta ; \quad I_B = \frac{I_c}{\beta} = \frac{8}{250}$$

$$V_{BB} = I_B R_B + V_{BE} + V_C^o ; \quad R_B = \frac{V_{BB} - V_{BE}}{I_B} = \frac{10 - 0,7}{8}$$

$$R_B = 290,625 \text{ k}\Omega$$