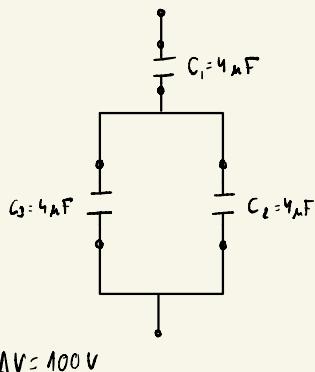



C_{AC} ? → Capacidad de todo el circuito

E_t ? → Energía total almacenada

Q_i ? → Carga almacenadas en cada uno de los condensadores


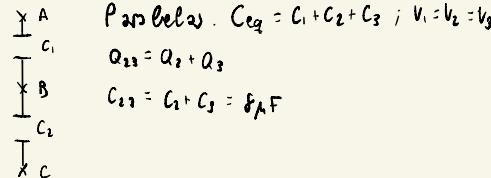
$$C = \frac{Q}{\Delta V} ; E = \frac{1}{2} CV^2 ; H = \frac{E}{V_{de}} = \frac{1}{2} E_0 \epsilon^2$$



$$\text{Paralelo} . C_{eq} = C_1 + C_2 + C_3 ; V_1 = V_2 = V_3$$

$$Q_{23} = Q_2 + Q_3$$

$$C_{23} = C_2 + C_3 = 8 \mu\text{F}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_{23}} \rightarrow C_{eq} = \frac{32}{12} = \frac{8}{3} \mu\text{F}$$

$$Q_{eq} = Q_1 = Q_{23}$$

$$V_{AC} = V_{23} + V_1$$


$$G = \frac{1}{2} CV^2 = \frac{1}{2} \cdot \frac{8}{3} \cdot (100)^2 \cdot 10^{-6} = \frac{4}{3} \cdot 10^{-2} \text{ J}$$

$$Q_1 = Q_{AC} = \frac{8}{3} \cdot 100 = \frac{800}{3} \mu\text{C}$$

$$Q_{AC} = Q_1 = Q_{23}$$

$$V_{BC} = \frac{Q_2}{C_3} = \frac{Q_2}{C_2} = \frac{800/3}{8} = \frac{100}{3} \text{ V}$$
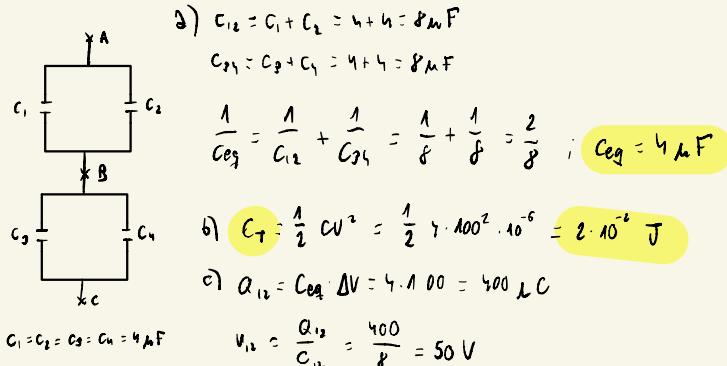
$$Q_2 = Q_3 = V_{BC} C_3 = \frac{100}{3} \cdot 4 = \frac{400}{3} \mu\text{C}$$




$$Q_1 = Q_2 = Q_3 = Q_4 = V_{12} \cdot C_1 = 50 \cdot 4 = 200 \mu C$$

Capaconditividade condensador?

$$\epsilon_R = 2,3$$

$$d = 0,3 \text{ nm}$$

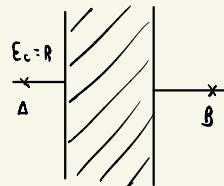
$$A = 400 \text{ cm}^2 = 4 \cdot 10^{-4} \text{ m}^2$$



$$C_0 = \frac{\epsilon_0 S}{d}$$

$$C = \epsilon_r C_0 = \frac{\epsilon_r \epsilon_0 S}{d}$$
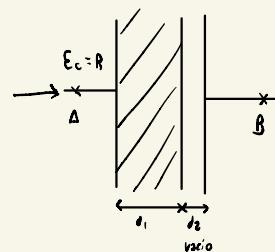
$$C_1 = \frac{\epsilon_r \epsilon_0 S \Delta}{d} = \frac{2,3 \cdot 8,82 \cdot 10^{-12} \cdot 4}{3 \cdot 10^{-4}}$$




$$d_1 = 0,215 \cdot 10^{-3} = 2,15 \cdot 10^{-4}$$

$$d_2 = (3 - 2,215) \cdot 10^{-3} = 7,85 \cdot 10^{-4}$$

$$C_1 = \frac{\epsilon_0 \epsilon_r S \cdot 10^{-2}}{(3 - d_2) \cdot 10^{-4}}$$


$$C_2 = \frac{\epsilon_0 S \cdot 10^{-2}}{d_1 \cdot 10^{-4}}$$
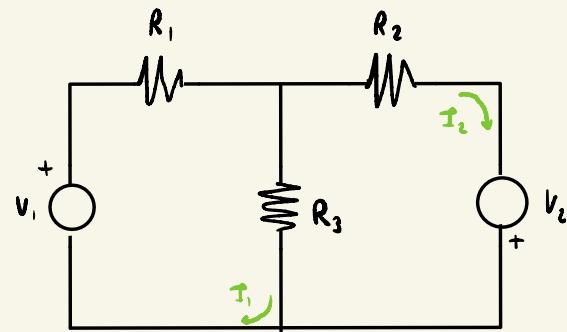
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$



$$\begin{aligned} V_1 &= I_1 R_1 + (I_1 - I_2) R_3 = I_1 R_1 + I_1 R_3 - I_2 R_3 = I_1 (R_1 + R_3) - I_2 R_3 \\ V_2 &= I_2 R_2 + (I_2 - I_1) R_3 = I_2 R_2 + I_2 R_3 - I_1 R_3 = I_2 (R_2 + R_3) - I_1 R_3 \end{aligned} \quad \left. \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \begin{pmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{pmatrix} \right\}$$

$$I_1 = \frac{\begin{vmatrix} V_1 & -R_3 \\ V_2 & R_2 + R_3 \end{vmatrix}}{\begin{vmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{vmatrix}} \quad I_2 = \frac{\begin{vmatrix} R_1 + R_3 & V_1 \\ -R_3 & V_2 \end{vmatrix}}{\begin{vmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{vmatrix}} \rightarrow \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \begin{pmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{pmatrix}$$

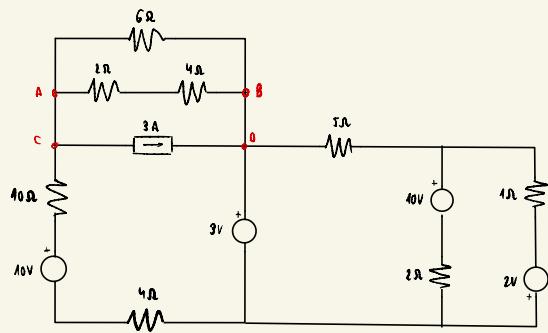

$$R_{AB} = 2 + 4 = 6 \Omega$$


$$\frac{1}{R_{CD}} = \frac{1}{6} + \frac{1}{6} = \frac{1}{3} \quad ; \quad R_{CD} = 3 \Omega$$



$$V_{ce} - RI = 9 - 3 = 6V$$

$$\begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} \rightarrow \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 10+2 \\ 10-2 \\ 10+2 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

$$I_1 = \frac{\begin{vmatrix} 0 & 0 \\ 10 & 2 \end{vmatrix}}{\begin{vmatrix} 10 & 2 & 2 \\ 10 & 0 & 0 \\ 0 & 2 & 2 \end{vmatrix}} = 0,94A$$

$$P_1 = 4 \cdot (0,94)^2 = 3,58W$$

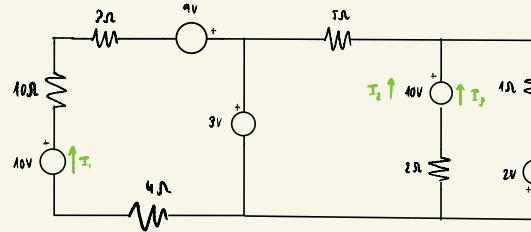

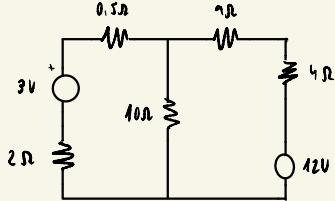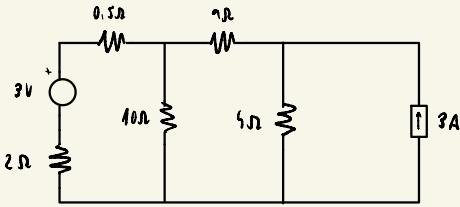


$$V = RI = 4 \cdot 3 = 12V$$

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \rightarrow \begin{pmatrix} 3 \\ 12 \end{pmatrix} = \begin{pmatrix} 40+2+0.5 & 10 \\ 10 & 40+9+4 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$I_1 = \frac{\begin{vmatrix} 3 & 10 \\ 12 & 23 \end{vmatrix}}{\begin{vmatrix} 42.5 & 10 \\ 16.5 & 23 \end{vmatrix}}$$

$$I_2 = \frac{\begin{vmatrix} 42.5 & 10 \\ 16.5 & 23 \end{vmatrix}}{\begin{vmatrix} 42.5 & 40 \\ 16.5 & 23 \end{vmatrix}}$$


Método de tensiones de nodos

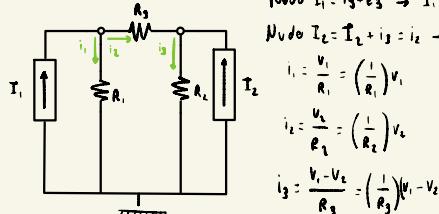

$$\begin{aligned}
 \text{Nodo } T_1: i_3 + i_2 &\rightarrow I_1 = \left(\frac{1}{R_1}\right)V_1 + \left(\frac{1}{R_3}\right)(V_1 - V_2) \rightarrow I_1 = G_1 V_1 + G_2 V_1 - G_3 V_2 \\
 \text{Nodo } T_2: I_2 + i_2 &= i_1 \rightarrow I_2 = i_1 - i_3 \rightarrow I_2 = \left(\frac{1}{R_2}\right)V_2 - \left(\frac{1}{R_3}\right)(V_1 - V_2) \rightarrow I_2 = G_2 V_2 - G_3 V_1 + G_3 V_2
 \end{aligned} \quad \left. \begin{array}{l} I_1 = V_1(G_1 + G_3) - V_2 G_3 \\ I_2 = -V_1 G_3 + V_2 (G_2 + G_3) \end{array} \right\}$$

$$\begin{aligned}
 i_1 &= \frac{V_1}{R_1} = \left(\frac{1}{R_1}\right)V_1 \\
 i_2 &= \frac{V_2}{R_2} = \left(\frac{1}{R_2}\right)V_2 \\
 i_3 &= \frac{V_1 - V_2}{R_3} = \left(\frac{1}{R_3}\right)(V_1 - V_2)
 \end{aligned}$$
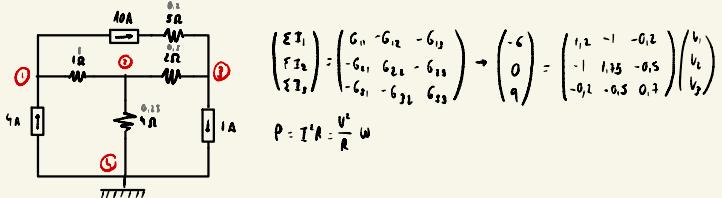
$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} G_1 + G_3 & -G_3 \\ -G_3 & G_2 + G_3 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$




O inversor de R


$$V_1 = \frac{\begin{vmatrix} -1,2 & -6 & -0,2 \\ -1 & 0 & -0,2 \\ -6,12 & 0,2 & 0,2 \end{vmatrix}}{\begin{vmatrix} 1,2 & -1 & -0,2 \\ -1 & 1,15 & -0,5 \\ -6,15 & -0,5 & 0,2 \end{vmatrix}} = \frac{-6}{9}$$

$$P = I^2 R = \frac{V^2}{R} W$$

Método de superposición

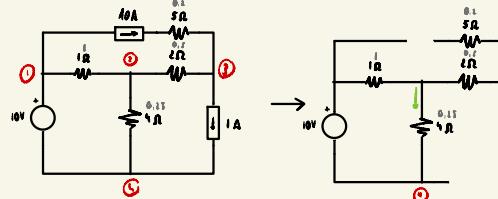
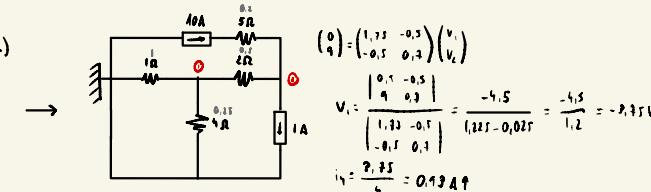
$$i_A = \frac{10}{\delta} = 2 \text{ A J (F. tensión)}$$



$$\begin{pmatrix} 0 \\ 1 \end{pmatrix} = \begin{pmatrix} 1.75 & -0.5 \\ -0.5 & 0.2 \end{pmatrix} \begin{pmatrix} V_L \\ V_L \end{pmatrix}$$



$$V_L = \frac{\begin{vmatrix} 1 & -0.5 \\ 1 & 0.2 \end{vmatrix}}{\begin{vmatrix} 1.75 & -0.5 \\ -0.5 & 0.2 \end{vmatrix}} = \frac{-4.5}{1.225 - 0.025} = \frac{-4.5}{1.2} = -3.75 \text{ V}$$

$$i_A = \frac{2.75}{0.1} = 0.1375 \text{ A}$$

$$I_{TH} = 2A(1) - 0.1375A(0) = 1.0125 \text{ A (L)}$$

$$P = i^2 R = (1.0125)^2 \cdot 0.1 = \dots$$

Método de Thevenin y Norton

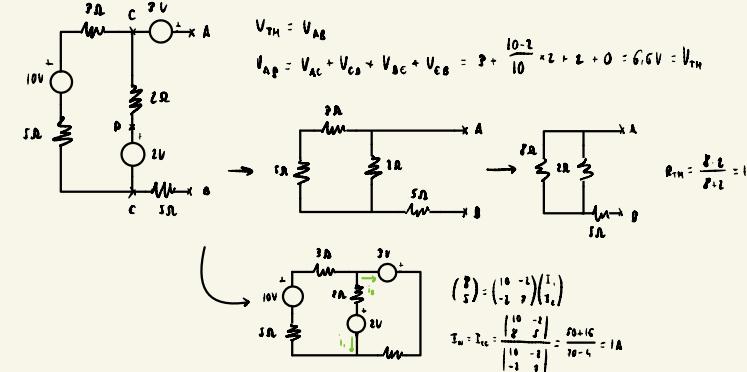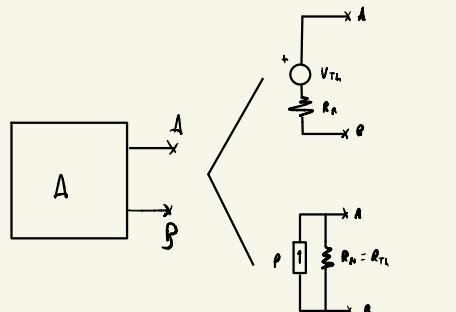


$$V_{AB} = V_{AC} + V_{CB} + V_{BC} + V_{EB} = 2 + \frac{10-2}{10} \times 2 + 2 + 0 = 6.6 \text{ V} = V_{TH}$$

$$R_{IN} = \frac{2 \cdot 2}{2+1} = 1.33 \Omega$$

$$\begin{pmatrix} 2 \\ 1 \end{pmatrix} = \begin{pmatrix} 10 & -1 \\ -1 & 1 \end{pmatrix} \begin{pmatrix} V_L \\ V_L \end{pmatrix}$$
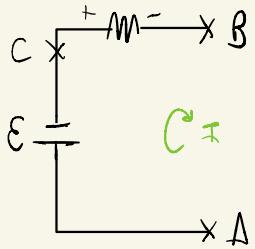
$$I_{TH} = I_{AB} = \frac{\begin{vmatrix} 10 & -1 \\ -1 & 1 \end{vmatrix}}{\begin{vmatrix} 10 & -1 \\ -1 & 1 \end{vmatrix}} = \frac{10-1}{10-1} = 1 \text{ A}$$




$$I_{CL} = \frac{E}{R} \quad E = I_{CC} R$$

\longleftrightarrow


$$R = r$$

$$V_{CB} = IR$$

$$V_{BC} = -IR$$

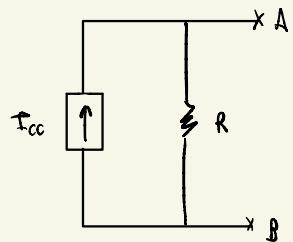


$$I_{CC} = \frac{E}{R}$$

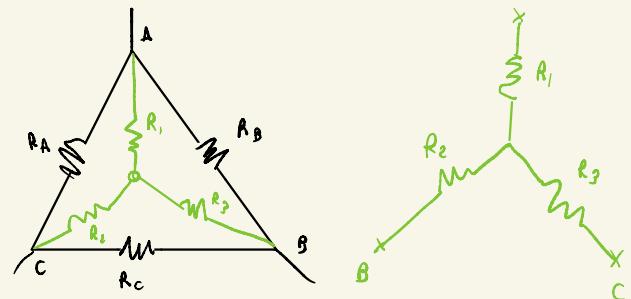

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$
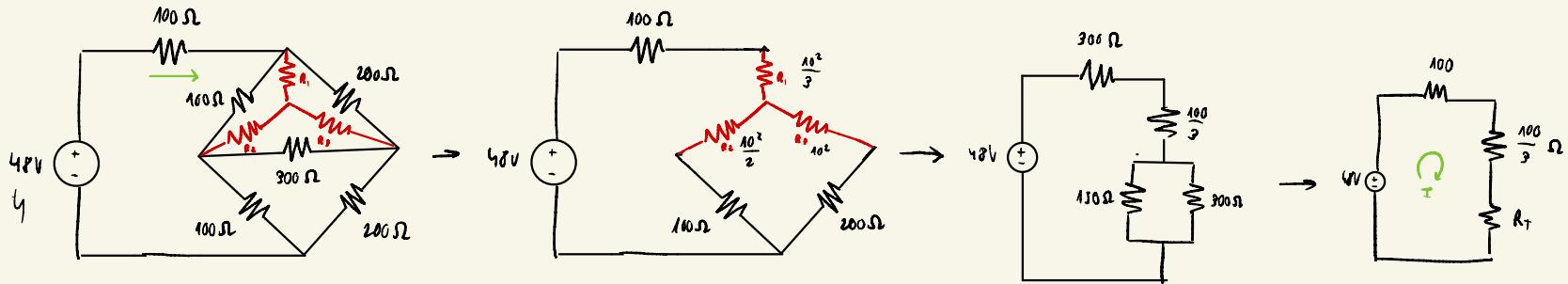
$$R_3 = \frac{R_B R_C}{R_A + R_B + R_C}$$



$$R_1 = \frac{2 \cdot 10^4}{6 \cdot 10^2} = \frac{1}{3} \cdot 10^2$$


$$R_2 = \frac{3 \cdot 10^4}{6 \cdot 10^2} = \frac{1}{2} \cdot 10^2$$

$$R_3 = \frac{6 \cdot 10^4}{6 \cdot 10^2} = 10^2$$

$$I = \frac{\Sigma E - \Sigma E' }{\Sigma R} = \frac{48}{100/3} = \frac{48 \cdot 3}{100}$$

$$R_T = \frac{150 \cdot 200}{450} = \frac{4500}{45} = 100 \Omega$$
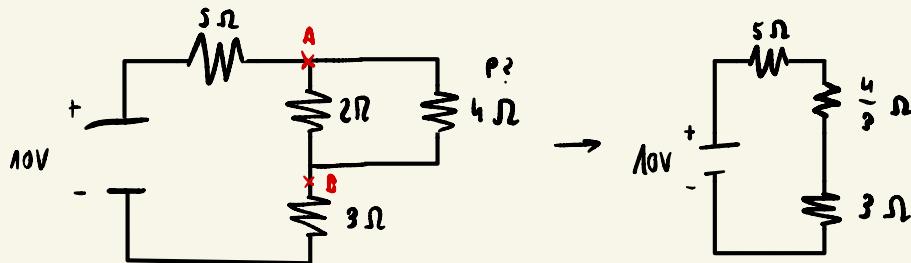
$$R_T = 200 + \frac{100}{3} = \frac{700}{3}$$




$$I = \frac{E}{\sum R} = \frac{10}{5+3+\frac{4}{3}} = \frac{10 \cdot 3}{18+9+4} = \frac{30}{28} \text{ A}$$

$$V_{AB} = R_{eq} \cdot \frac{30}{28} = \frac{4}{3} \cdot \frac{30}{28} = \frac{40}{28}$$

$$I = \frac{V}{R} = \frac{40/28}{4} = \frac{10}{28} \text{ A}$$

$$Q = I^2 R = 4 \left(\frac{10}{28} \right)^2 \text{ W}$$

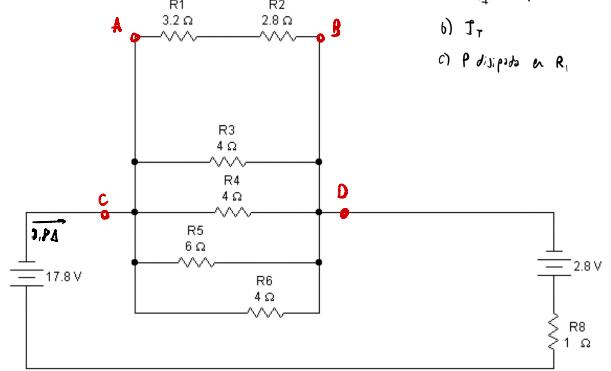9.- Completar el siguiente cuadro con el voltaje, la intensidad de corriente y la potencia eléctrica disipada por cada resistencia: a) R_{eq} del paralelo



$$a) R_{eq} = 2.8 + 3.2 = 6 \Omega$$


$$R_{eq} = \frac{1}{R_{eq}} = \frac{1}{\frac{1}{6} + \frac{1}{4} + \frac{1}{4} + \frac{1}{6} + \frac{1}{6}} = \frac{2}{6} + \frac{2}{3} = \frac{13}{12} \quad R_{eq} = \frac{12}{13} \Omega$$

$$b) I_T = \frac{\Delta E - E' E}{R_{eq}} = \frac{17.8 - 6.8}{1 + \frac{12}{13}} = \frac{15}{25/13} = 7.8 A$$

$$c) V_{eq} = I_T R_7 = 7.8 \cdot \frac{12}{13} = 7.2 V$$


$$I_2 = \frac{V_{eq}}{R_{eq}} = \frac{7.2}{6} A$$
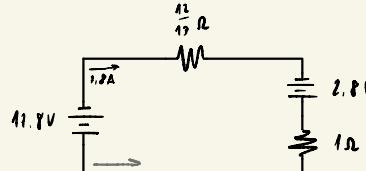
$$P_1 = I^2 R_1 = \left(\frac{7.2}{6}\right)^2 \cdot 2.2 = 9.6 W$$




a) En el circuito calcula la intensidad de la rama donde está $R = 3\Omega$
 así como las cantidades de calor disipado en los $R = 4\Omega$ en $t = 60s$

a) I_{R_2} b) $W_{R_2} t = 60s$

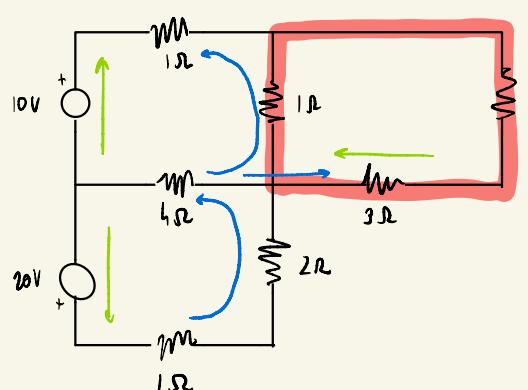

$$\left(\begin{matrix} \Sigma E_i \\ \Sigma E_i \end{matrix} \right) = \left(\begin{matrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{matrix} \right) \rightarrow \left(\begin{matrix} 10 \\ 20 \end{matrix} \right) = \left(\begin{matrix} 1 & 1 \\ 4 & 7 \end{matrix} \right)$$
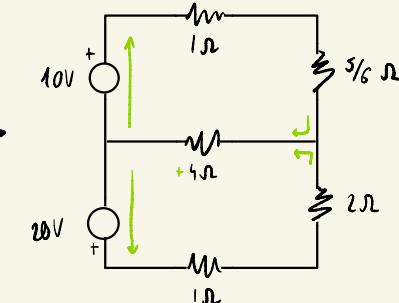
$$\frac{1}{R_{11}} + \frac{1}{R_{21}} = \frac{1}{5}$$



$$\left(\begin{matrix} \Sigma E_i \\ \Sigma E_i \end{matrix} \right) = \left(\begin{matrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{matrix} \right) \rightarrow \left(\begin{matrix} 10 \\ 20 \end{matrix} \right) = \left(\begin{matrix} 1 & 1 \\ 4 & 7 \end{matrix} \right)$$

$$I_1 = \frac{\begin{vmatrix} 10 & 1 \\ 20 & 7 \end{vmatrix}}{\begin{vmatrix} 1 & 1 \\ 4 & 7 \end{vmatrix}} = \frac{30 - 80}{6 - 16} = -0,4027 A \rightarrow \text{cambiar el sentido. } I_1 = 0,4027 A \uparrow$$

$$I_2 = \frac{\begin{vmatrix} 1 & 10 \\ 4 & 20 \end{vmatrix}}{\begin{vmatrix} 1 & 1 \\ 4 & 7 \end{vmatrix}} = \frac{-300}{6 - 16} = 3,09 A \downarrow$$

$$b) V_{AB} = I_1 \cdot R_{\text{ref}} = 0,4 \cdot \frac{5}{6} = \frac{1}{3} V$$

$$i_2 = \frac{V}{R_{\text{ref}}} = \frac{1/3}{5} = \frac{1}{15} A$$

$$b) I_{R_2} = I_2 - I_1 = 3,09 - 0,4 = 2,69 A$$


como tiene sentido del lado Mayor-Menor

$$P = I_{R_2}^2 R_{R_2} = 2,69^2 \cdot 4 = 28,9444 W$$

$$Q = P \cdot 0,24 \cdot t = 28,9444 \cdot 0,24 \cdot 60 = 416,1999$$




Circuitos de tensión en R3e

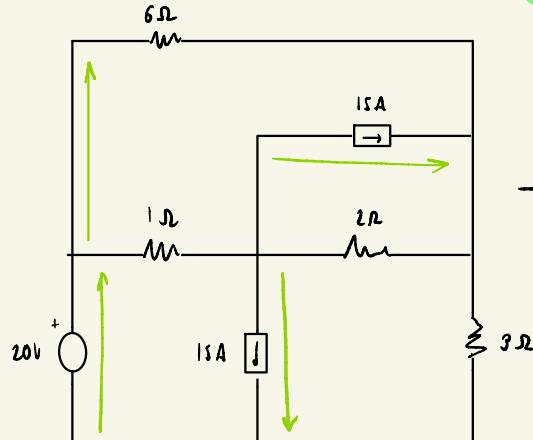


Superposición

1º eliminando f. intensidad

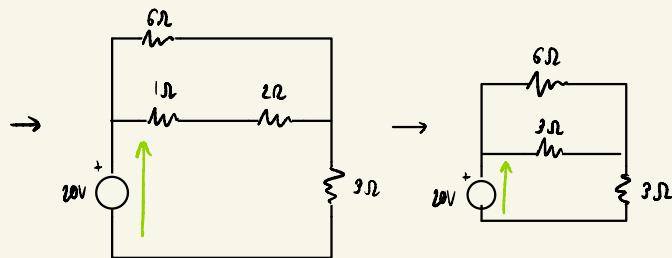

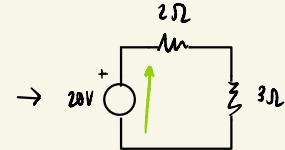
$$\frac{1}{R} = \frac{1}{6} + \frac{1}{3} = \frac{3}{6} = \frac{1}{2}$$



$$20V \xrightarrow{\quad} 3\Omega$$

2º eliminando f. tensión

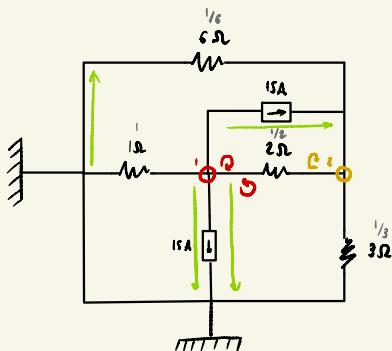

$$\begin{pmatrix} \sum I_1 \\ \sum I_2 \end{pmatrix} = \begin{pmatrix} G_{11} & -G_{12} \\ -G_{21} & G_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

$$\begin{pmatrix} -30 \\ 15 \end{pmatrix} = \begin{pmatrix} 1,5 & -0,5 \\ -0,5 & 1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

$$V_2 = \frac{\begin{vmatrix} 1,5 & -30 \\ -0,5 & 15 \end{vmatrix}}{\begin{vmatrix} 1,5 & 15 \\ -0,5 & 1 \end{vmatrix}} = 6V$$



$$I_2 = \frac{6}{3} = 2A$$

$$I_T = 4 + 2 = 6A$$


$$V_{3e} = 6 \cdot 3 = 18V$$

a) Calcular equivalente entre A y B

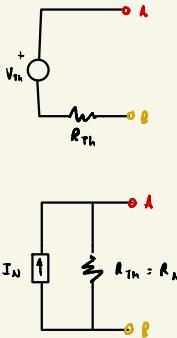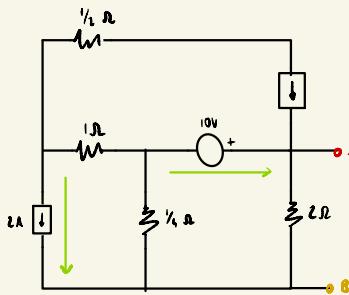b) Potencia disipada en $R = 4\Omega$ que se colocara entre A y B



1º eliminando f. tensión

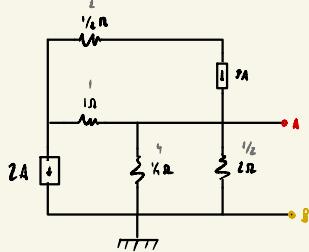

$$\begin{pmatrix} \sum I_1 \\ \sum I_2 \end{pmatrix} = \begin{pmatrix} G_{11} & -G_{12} \\ -G_{21} & G_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$




$$\begin{pmatrix} 3 \\ -2 \end{pmatrix} = \begin{pmatrix} 5,5 & -3 \\ -3 & 2 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

$$V_1 = \frac{\begin{vmatrix} 3 & -3 \\ -2 & 2 \end{vmatrix}}{\begin{vmatrix} 5,5 & -3 \\ -3 & 2 \end{vmatrix}} = \frac{3}{7,5} = 0,4V$$

$$V_{th} = V_{AB} + V_1 = \frac{P_0}{9} + 0,4 = 9,28$$

Superposición

1º eliminando f. intensidad

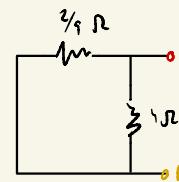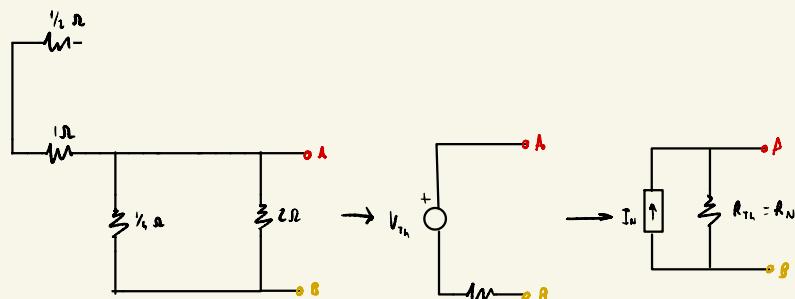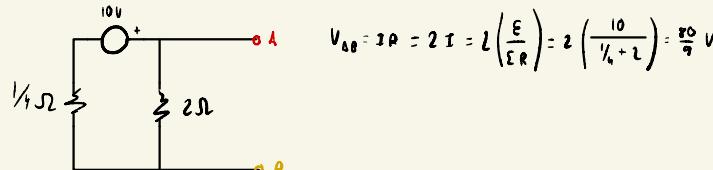

$$R_{th} = \frac{1}{\frac{1}{1/4} + \frac{1}{2}} = \frac{1}{9} \Omega$$

$$V_{th} = I R = 1 \cdot \frac{2}{9} = 9,3V$$

$$P = I^2 R = \left(\frac{9,3}{1 + \frac{2}{9}} \right)^2 \cdot 4 = 19,4063 W$$

a) Calcular equivalente entre A y B

b) Potencia disipada en $R = 4\Omega$ que se colocara entre A y B

